






**9.16** [M] Tree depth for carry-save reduction is analyzed in this problem.

(a) How many 3-2 reduction levels are needed to reduce 16 summands to 2 using a pattern similar to that shown in Figure 9.19?

(b) Repeat part (a) for reducing 32 summands to 2 to show that the claim of 8 levels in Section 9.5.3 is correct.

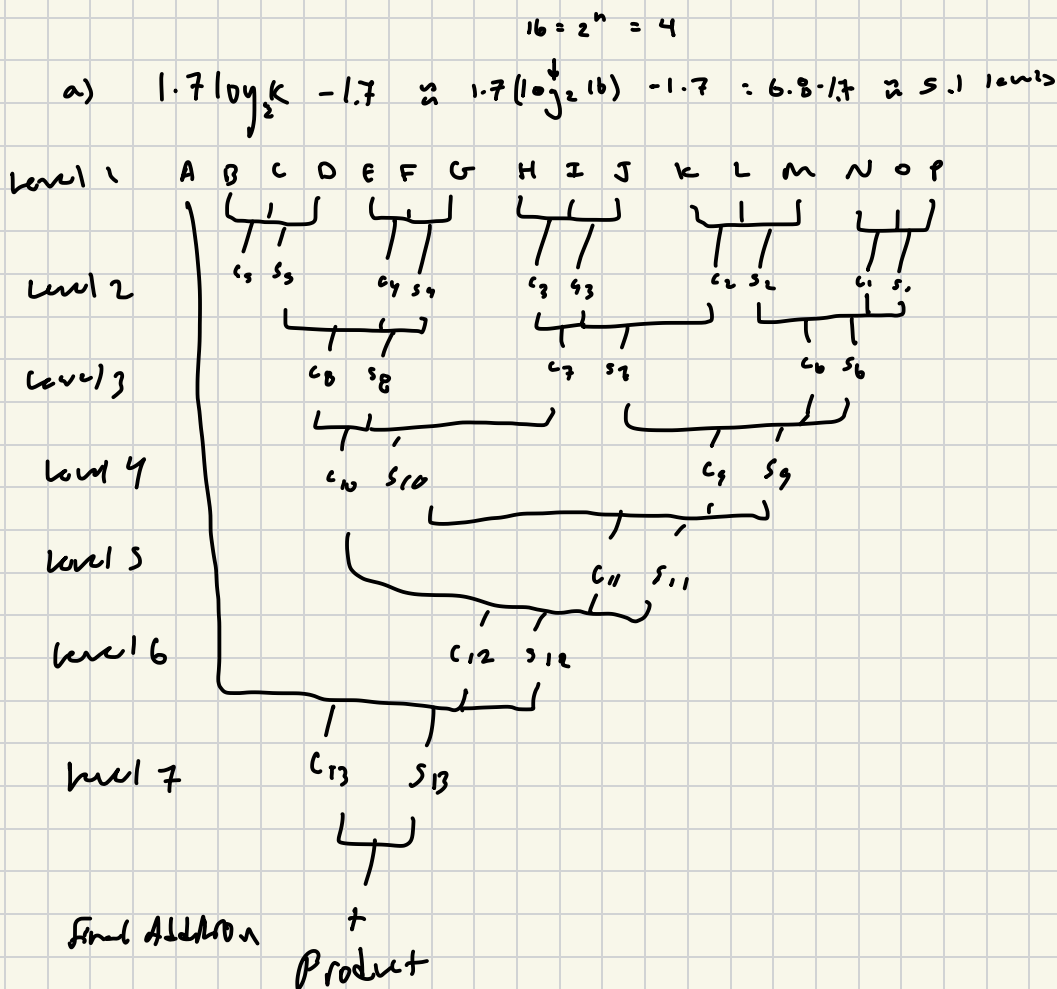(c) Compare the exact answers in parts (a) and (b) to the results obtained by using the approximation developed in Example 9.3 in Section 9.10.




7 reducing levels are required before final addition can be reached

**9.16 [M]** Tree depth for carry-save reduction is analyzed in this problem.


- (a) How many 3-2 reduction levels are needed to reduce 16 summands to 2 using a pattern similar to that shown in Figure 9.19?
- (b) Repeat part (a) for reducing 32 summands to 2 to show that the claim of 8 levels in Section 9.5.3 is correct.
- (c) Compare the exact answers in parts (a) and (b) to the results obtained by using the approximation developed in Example 9.3 in Section 9.10.

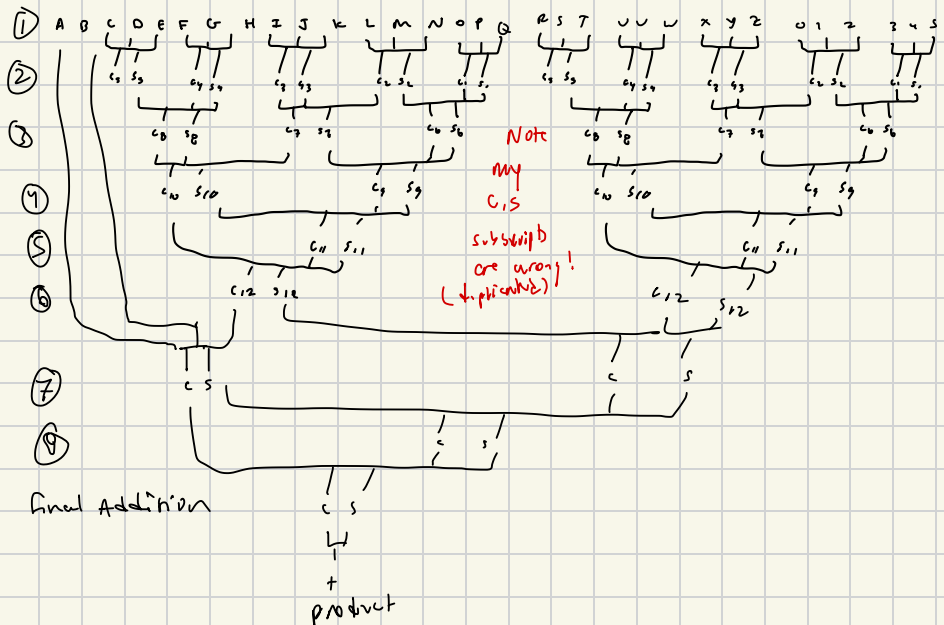b) claim 8 levels,  $k=32$  ✓  $32 = 2^n$   $n=5$

$$1.7 \log_2 k - 1.7 \rightarrow 1.7 \log_2(32) - 1.7 = 1.7 \cdot 5 - 1.7 \approx 6.8 \text{ levels}$$



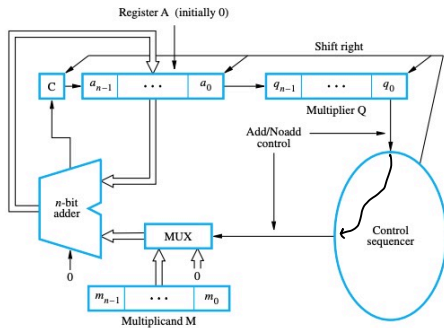**9.20 [M]** Show how the multiplication and division operations in Problem 9.19 would be performed by the hardware in Figures 9.7a and 9.23, respectively, by constructing charts similar to those in Figures 9.7b and 9.25.



(a) Register configuration

		M							
		1 1 0 1							
C	A	0 0 0 0				1 0 1 1			
0	0 1 1 0	1 0 1 1							
0	0 1 1 0	1 1 0 1							
1	0 0 1 1	1 1 0 1							
0	1 0 0 1	1 1 1 0							
0	1 0 0 1	1 1 1 0							
0	0 1 0 0	1 1 1 0							
1	0 0 0 1	1 1 1 1							
0	1 0 0 0	1 1 1 1							
		Product							

(b) Multiplication example

Figure 9.7 Sequential circuit binary multiplier.

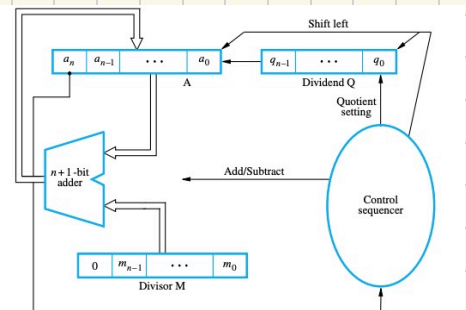


Figure 9.23 Circuit arrangement for binary division.

Initially	0 0 0 0 0	1 0 0 0		
Shift	0 0 0 1 1			
Subtract	0 0 0 0 1	0 0 0		
Set $q_0$	1 1 1 0 1	0 0 0 0		
Shift	1 1 1 0 0	0 0 0		
Add	0 0 0 1 1	0 0 0 0		
Set $q_0$	1 1 1 1 1	0 0 0 0		
Shift	1 1 1 1 0	0 0 0		
Add	0 0 0 1 1	0 0 0		
Set $q_0$	0 0 0 0 1	0 0 0 1		
Shift	0 0 0 1 0	0 0 1		
Subtract	1 1 1 0 1	0 0 1 1		
Set $q_0$	1 1 1 1 1	0 0 1 1 0		
			Quotient	
Add	1 1 1 1 1			
	0 0 0 1 1			
	0 0 0 1 0			
			Remainder	
			Restore remainder	

Figure 9.25 A non-restoring division example.

Sequential circuit binary multiplier:

- ~ multiplication of 2 n-bit #
- ~ sequential  $\rightarrow$  n-bit add

uses n-bit adder n times for serial addition performed by ripple carry adders

\* A K Q are shift registers holding PPs

multiplicand generates  $q_i$  signal for add/no add

$q_i = 0$  : Select 0

$q_i = 1$  : select multiplicand M to be added

start: load multiplier into Register Q

- M, C, A cleared (0)

@ end of each cycle,

C, A, Q shift right to generate PP:

use  $q_i$  @ LSA.

problem solved on next page

**9.20** [M] Show how the multiplication and division operations in Problem 9.19 would be performed by the hardware in Figures 9.7a and 9.23, respectively, by constructing charts similar to those in Figures 9.7b and 9.25.

9.19: using manual methods, perform the operations

$$A \times B$$

$$A \div B$$

on the 5 bit unsigned numbers

$$A = 10101$$

$$B = 00101$$

		M			
		10101		} initial config	
		00000	00101		
		C	A	Q	
cycles					
1	{	0	10101	00101	Add shift
		0	01010	10010	
2	{	0	01010	10010	no add shift
		0	00101	01001	
3	{	0	00101	01001	no add shift
		0	00010	00100	
4	{	0	10111	00100	Add shift
		0	01011	10010	
5	{	0	01011	10010	no add shift
		0	00101	11001	

product

A ÷ B

initial 00000 10101  
00101

shift 00010 01010 } 1  
no add 1101  
set q<sub>4</sub> 11100 01010

shift 1100  
add 00101  
set q<sub>3</sub> 00001 10100 } 2

shift 00010 01001  
sub 11011  
set q<sub>2</sub> 11101 01001 } 3

shift 11101 10010  
add 00101  
set q<sub>1</sub> 00010 10010 } 4


shift 00010 00101  
sub 11011  
set q<sub>0</sub> 11111 00101 } 5

Add 11111  
no add 00101  
remainder 00100

remainder

**9.22** [D] Consider a 16-bit, floating-point number in a format similar to that discussed in Problem 9.21, with a 6-bit exponent and a 9-bit mantissa fraction. The base of the scale factor is 2 and the exponent is represented in excess-31 format.

 (a) Add the numbers  $A$  and  $B$ , formatted as follows:



Give the answer in normalized form. Remember that an implicit 1 is to the left of the binary point but is not included in the  $A$  and  $B$  formats. Use rounding as the truncation method when producing the final mantissa.

(b) Using decimal numbers  $w$ ,  $x$ ,  $y$ , and  $z$ , express the magnitude of the largest and smallest (nonzero) values representable in the preceding normalized floating-point format. Use the following form:

$$\text{Largest} = w \times 2^x$$

$$\text{Smallest} = y \times 2^{-z}$$

#### Add/Subtract Rule

1. Choose the number with the smaller exponent and shift its mantissa right a number of steps equal to the difference in exponents.
2. Set the exponent of the result equal to the larger exponent.
3. Perform addition/subtraction on the mantissas and determine the sign of the result.
4. Normalize the resulting value, if necessary.

Multiplication and division are somewhat easier than addition and subtraction, in that no alignment of mantissas is needed.

$A =$ 

0	100001	111111110
---	--------	-----------

  
 $B =$ 

0	011111	001010101
---	--------	-----------

Above  $A$ : 1 2 3 4 5 6 (over 100001), 1 2 3 4 5 6 7 8 9 (over 111111110)  
 Above  $B$ : 0 1 (over 011111), 6 5 4 3 2 1 (over 001010101)

Difference in exponents is 31. Shift  $B$  mantissa right by 31 bits.

$B =$ 

0	011111	001010101
---	--------	-----------

  
 Shift right by 31 bits.

b) values representable:  $1. \text{mantissa} \times 2^{\text{exponent}}$

largest:

$$63 - 31 = 32 \rightarrow 1.11111111$$

$$\text{mantissa} = 1 + \frac{17}{32} = \frac{49}{32} \approx 1.53125$$

$$\text{largest} = 1.53125 \times 2^{32}$$

smallest:

$$0 - 31 = -31 \rightarrow 1.00000000$$

$$\text{smallest} = 1.0 \times 2^{-31}$$

15-bit

Mantissa:  $B = 1.M = 1.b_1 b_2 b_3 \dots b_{15}$

↓

normalized!

$$\text{val: } V(B) = 1 + 2^1(b_1) + 2^2(b_2) + \dots + 2^{15}(b_{15})$$

range 11-bit exponents:  $1 \leq E' \leq 2046$

Special

2047 Special

a) Calculation

①  $B_{\text{exp}} \neq A_{\text{exp}}$

difference:  $32 - 31 = 1$

8 mantissa shifts right twice

$$0.010010101 \approx 0.291015625$$

② larger exponent is 2

$$A: 1.11111110 \approx 1.99609375$$

$$③ + B: 0.010010101_2 \approx 0.291015625$$

$$\approx 2.297109375 > 2$$

thus needing normalization

④ shift left by 2  $\approx 1.1435546875$

convert back  $\rightarrow (1.00100100)_2$

new exponent:  $31 + 2 = 33 \rightarrow 1000101$

$$A+B = 0.100010001001001001$$